

# HKN EE42/100

## MT1 Review

Jyo Shim  
Paroma Varma  
Riyaz Faizullahoy

# Nodal Analysis

## Step 1:


- a) Identify all extraordinary nodes (connection point between at least 3 branches )
- b) Select one as ground
- c) Assign node voltage names to others

## Step 2:

- a) Apply KCLs at the nodes

## Step 3:

- a) Solve to determine unknowns

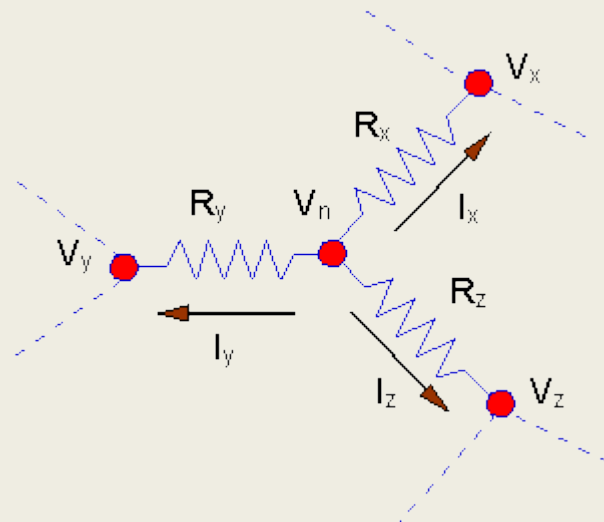


$$\frac{V_n - V_y}{R_y} + \frac{V_n - V_x}{R_x} + \frac{V_n - V_z}{R_z} = 0$$

# Nodal Analysis
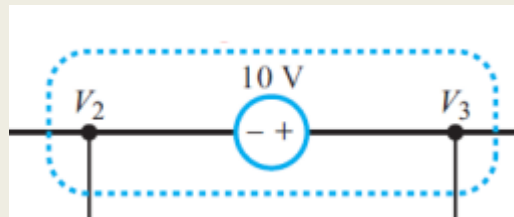
## Supernodes!

If we have a source between two nodes, we can “combine” them into a supernode!




We use the voltage difference to relate  $V_3$  and  $V_2$ :

$$V_3 - V_2 = 10 \text{ V}$$
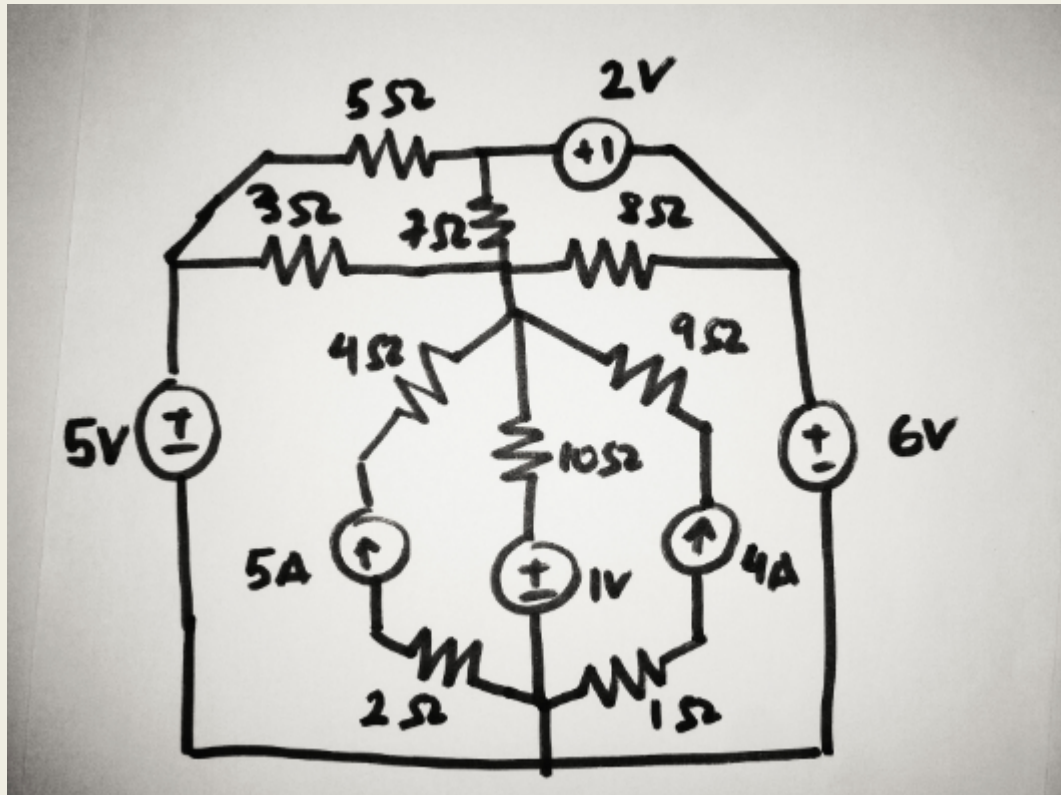
# Nodal Analysis

Let's put it all together!

Find the nodal analysis equation(s) to get voltages at each node!



# Mesh Analysis

## Step 1:


a) Identify all loops (meshes)

## Step 2:

a) Apply KVL on the loops

## Step 3:


a) Solve to determine unknowns

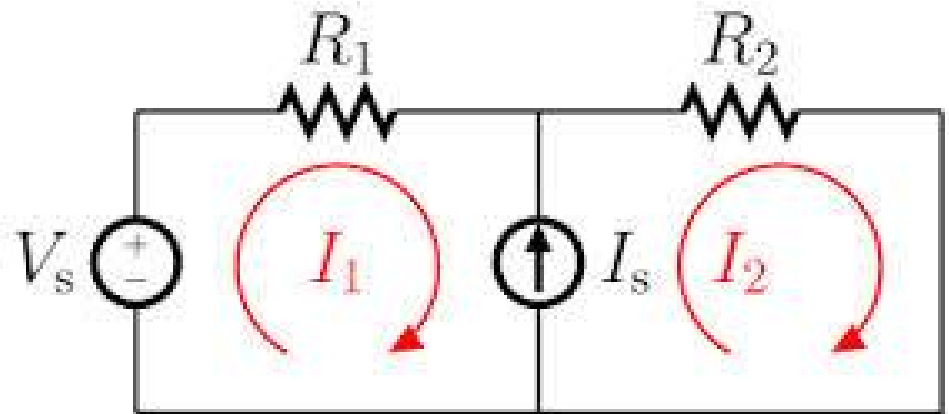

**We have a supermesh, where is it?**

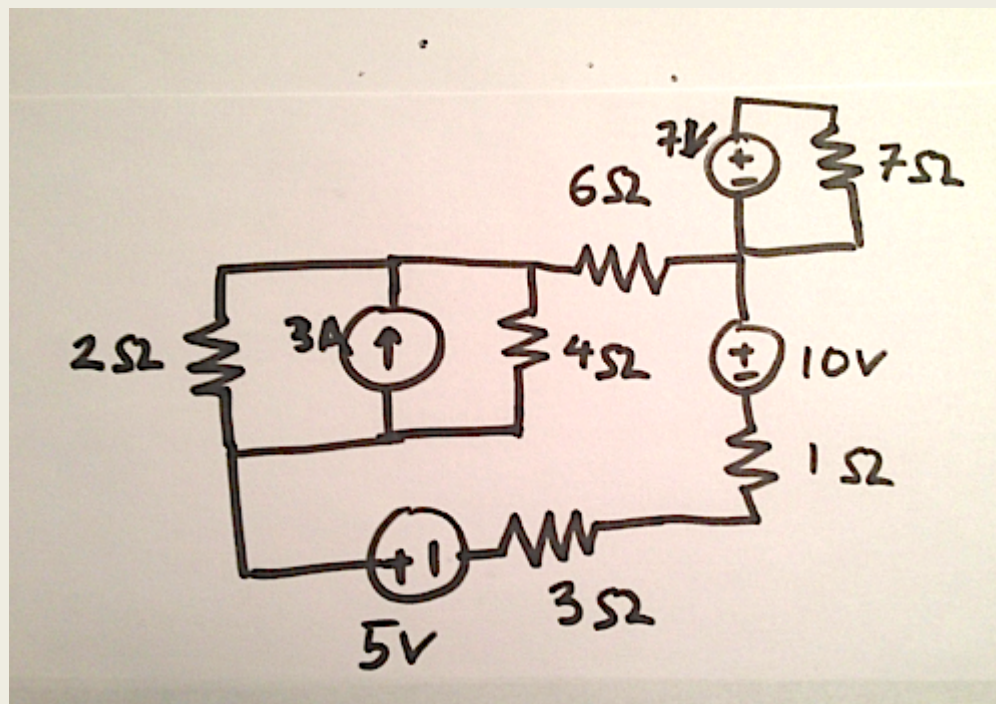
# Mesh Analysis

Find the mesh equations for this circuit!


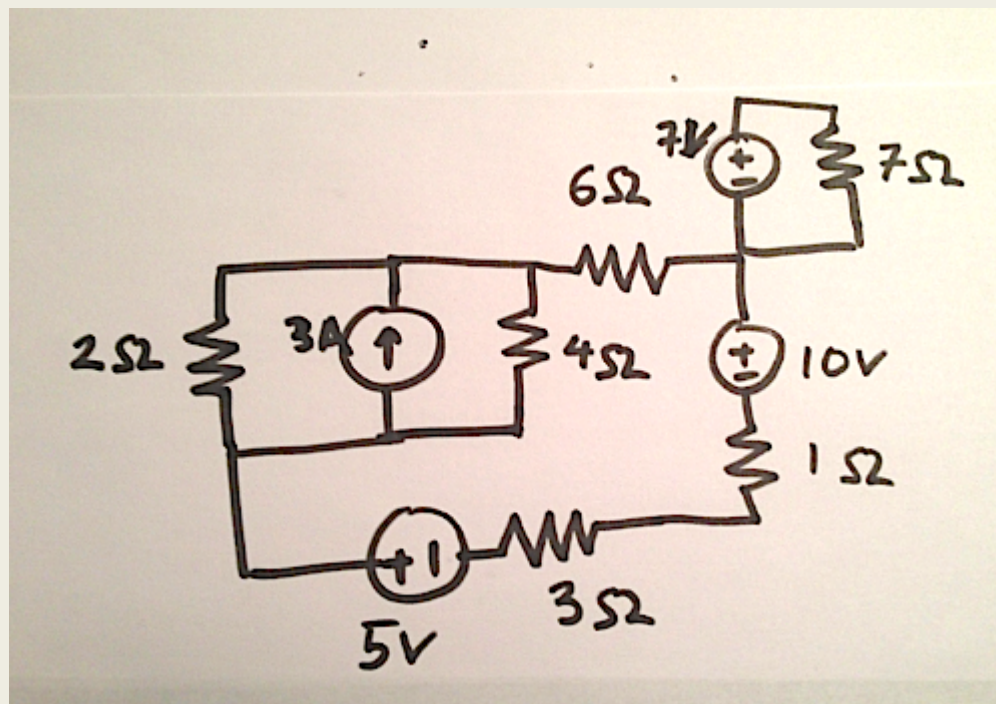
# Mesh Analysis

Find the mesh equations for this circuit!




# Dependent Sources

The values for the dependent source depend on values elsewhere in the circuit!

In this scenario:  $V_{\text{dep}} = 6I_x$ ,  $I_{\text{dep}} = 2I_y$

(could depend on voltages too)

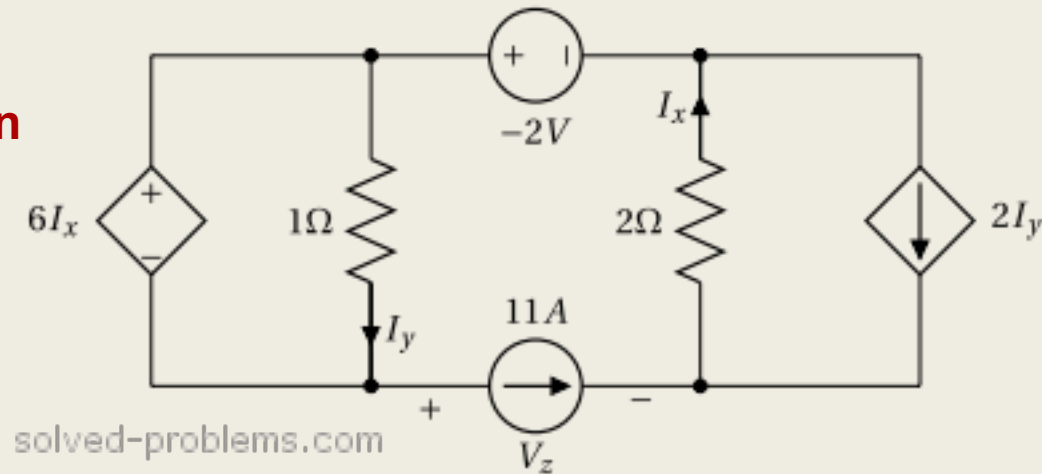




# Superposition

Analysis by superposition:

1. Select 1 independent source to keep, and turn off the rest:
  - a. Short independent voltage sources
  - b. Open independent current sources
2. Solve the circuit using KVL or KCL
3. Repeat for every independent source
4. The currents and voltages of the entire circuit is equal to the sum of the currents and voltages solved in (2.) for each source

# Superposition


Analysis by superposition:

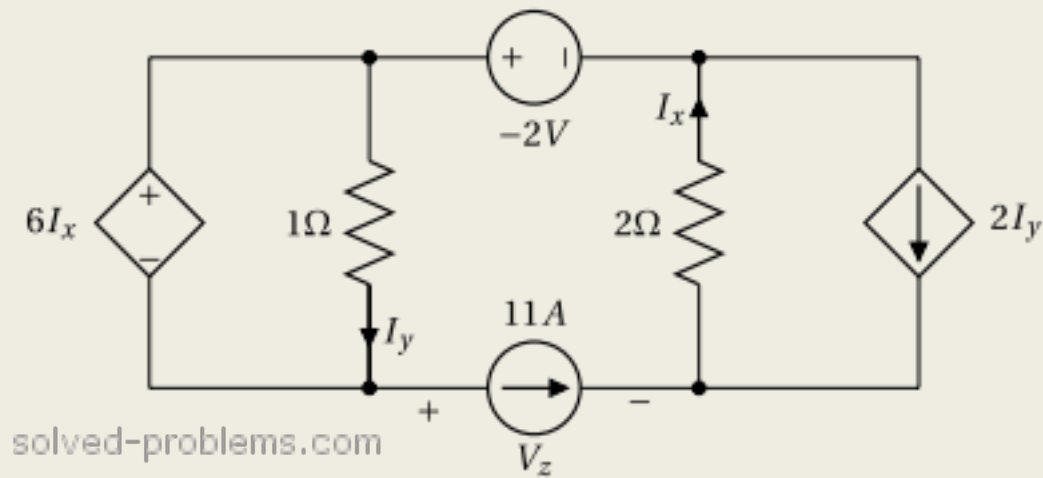

# Superposition

Analysis by superposition:

$$6I_x = 1 * I_y$$

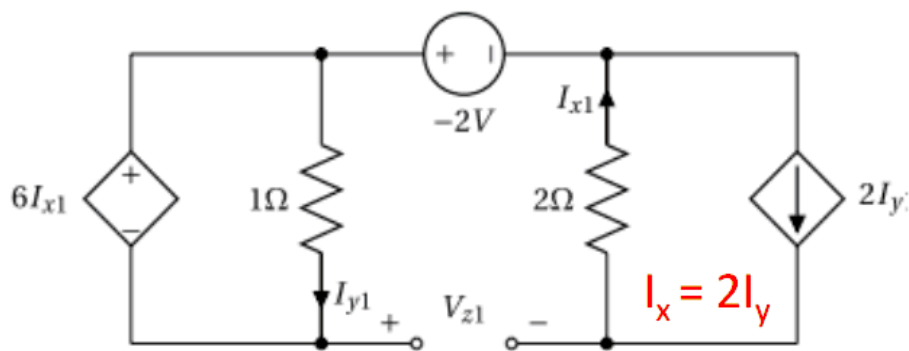

1. Turn off independent current source


2. Replace with open circuit

Since  $I_x$  and  $I_y$  are 0, there is no voltage drop across the resistors

$$I_x = 0 \quad I_y = 0 \quad V_z = -2V$$

# Superposition

Analysis by superposition:

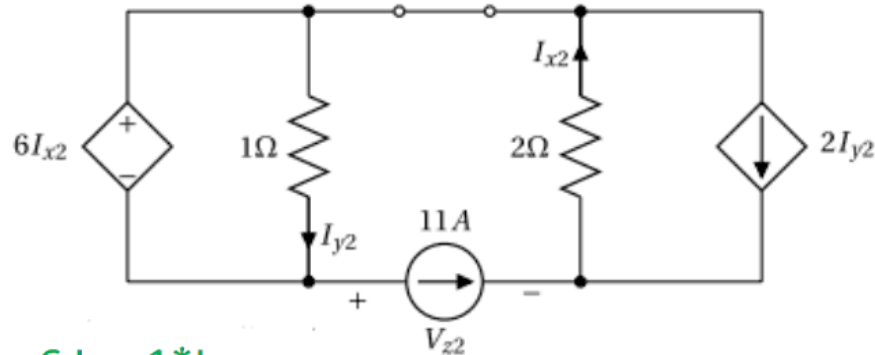

$$6I_x = 1 \cdot I_y$$

$$11A + 2I_y = I_x$$


$$2I_x + 1I_y + V_z = 0$$

1. Turn off independent voltage source
2. Replace with short circuit

$$I_x = -1A \quad I_y = -6A \quad V_z = 8V$$

# Superposition

Analysis by superposition:

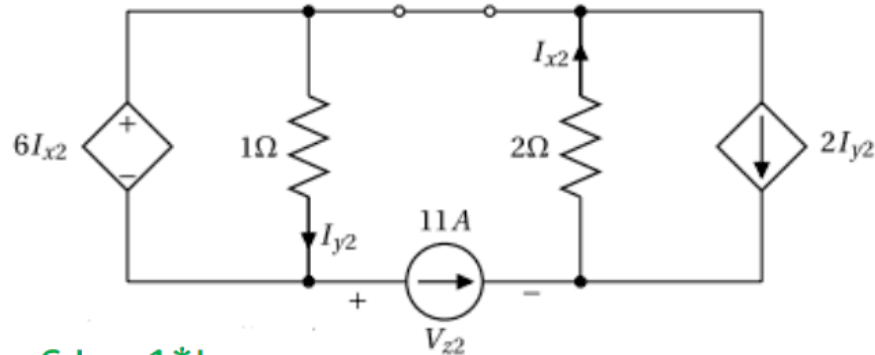

$$6I_x = 1 \cdot I_y$$

$$11A + 2I_y = I_x$$


$$2I_x + 1I_y + V_z = 0$$

1. Turn off independent voltage source
2. Replace with short circuit

$$I_x = -1A \quad I_y = -6A \quad V_z = 8V$$

# Superposition

Analysis by superposition:

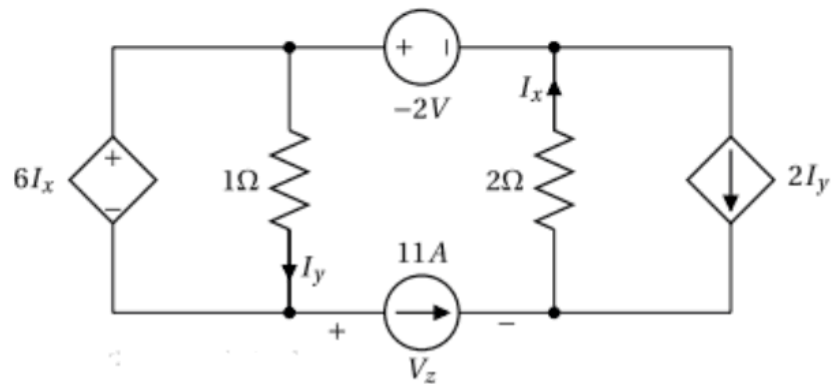

$$I_y = I_y + I_y = 0 + (-6A) = -6A$$

$$I_x = I_x + I_x = 0 + (-1A) = -1A$$

$$V_z = V_z + V_z = (-2V) + (8V) = 6V$$